

Digital Logic Design

Chapter 7 – Register & Register Transfers(I)

Registers, Micro-operations & Implementations

浙江大学计算机学院 王总辉

zhwang@zju.edu.cn

<http://course.zju.edu.cn>

2021年10月



Overview

- **Part 1 - Registers, Microoperations and Implementations**
 - Registers and load enable
 - Register transfer operations
 - Microoperations - arithmetic, logic, and shift
 - Microoperations on a single register
 - Multiplexer-based transfers
 - Shift registers
- **Part 2 - Counters, Register Cells, Buses, & Serial Operations**
- **Part 3 – Control of Register Transfers**




Registers

- Register – a **collection** of binary storage elements
- In theory, a register is sequential logic which can be defined by a state table
- More often, think of a register as storing a vector of binary values
- Frequently used to perform simple data storage and data movement and processing operations

 Example: 2-bit Register

- How many states are there?
- How many input combinations?
Output combinations?
- What is the *output function*?
- What is the *next state function*?
- Moore or Mealy?



State Table:

Current State	Next State A1(t+ 1) A0(t+ 1) For In1 In0 =	Output (=A1 A0)
A1 A0	00 01 10 11	Y1 Y0
0 0	00 01 10 11	0 0
0 1	00 01 10 11	0 1
1 0	00 01 10 11	1 0
1 1	00 01 10 11	1 1

- What are the *quantities* above for an n -bit register?

Register Design Models

- Due to the large numbers of states and input combinations as n becomes large, the state diagram/state table model is not feasible!
- What are methods we can use to design registers?
 - Add predefined combinational circuits to registers
 - Example: To count up, connect the register flip-flops to an incrementer
 - Design *individual cells* using the state diagram/state table model and combine them into a register
 - A 1-bit cell has just two states
 - Output is usually the state variable




Register Storage

- **Expectations:**
 - ❑ A register can store information for multiple clock cycles
 - ❑ To “store” or “load” information should be controlled by a signal
- **Reality:**
 - ❑ A D flip-flop register loads information on every clock cycle
- **Realizing expectations:**
 - ❑ Use a signal to *block* the clock to the register,
 - ❑ Use a signal to control *feedback* of the output of the register back to its inputs, or
 - ❑ Use other SR or JK flip-flops, that for (0,0) applied, store their state
- **Load is a frequent name for the signal that controls register storage and loading**
 - ❑ Load = 0: Load the values on the data inputs
 - ❑ Load = 1: Store the values in the register

Registers with Clock Gating

 - The **Load** signal enables the clock signal to pass through if 0 and prevents the clock signal from passing through if 1.
- Example: For Positive Edge-Triggered or Negative Pulse Master-Slave Flip-flop:



Gated Clock to FF

- What logic is needed for gating?
- **What is the problem?**

$$\text{Gated Clock} = \text{Clock} + \overline{\text{Load}}$$

Clock Skew of gated clocks with respect to clock or each other

Registers with Load-Controlled Feedback



- **A more reliable way to selectively load a register:**


- ❑ Run the clock continuously, and
- ❑ Selectively use a load control to change the register contents.

- **Example: 2-bit register with Load Control:**

- For Load = 0, loads register contents (hold current values)


- For Load = 1, loads input values (load new values)

 - Hardware more complex than clock gating, but free of timing problems




Register Transfer Operations

 - **Register Transfer Operations** – The movement and processing of data stored in registers



- **Three basic components:**
 - ❑ Set of registers
 - ❑ Operations
 - ❑ control of operations
- **Elementary Operations** -- load, count, shift, add, bitwise "OR", etc.
 - ❑ Elementary operations called *microoperations*


Register Notation

 

- Letters and numbers – denotes a register (ex. R2, PC, IR)
- Parentheses () – denotes a range of register bits (ex. R1(1), PC(7:0), PC(L))
- Arrow (\leftarrow) – denotes data transfer (ex. $R1 \leftarrow R2$, $PC(L) \leftarrow R0$)
- Comma – separates parallel operations
- Brackets [] – Specifies a memory address (ex. $R0 \leftarrow M[AR]$, $R3 \leftarrow M[PC]$)

Conditional Transfer

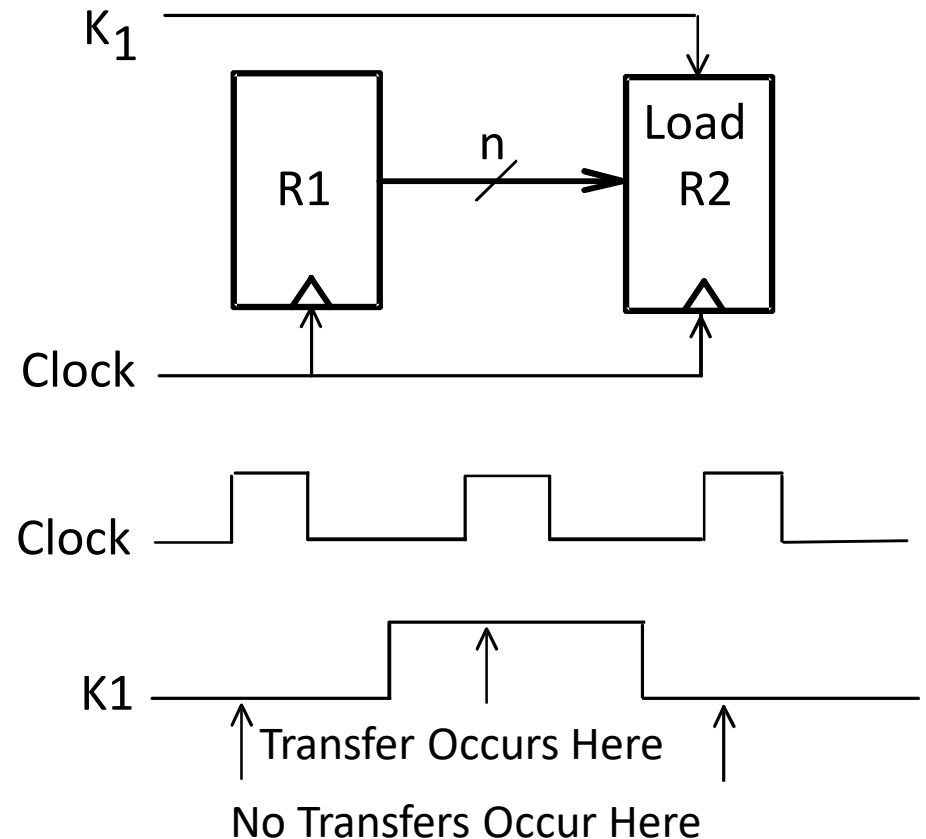- If $(K1 = 1)$ then $(R2 \leftarrow R1)$ is shortened to
 $K1: (R2 \leftarrow R1)$
where $K1$ is a control variable specifying a conditional execution of the microoperation.



Microoperations

- **Logical Groupings:**

- ❑ Transfer - move data from one register to another
- ❑ Arithmetic - perform arithmetic on data in registers
- ❑ Logic - manipulate data or use bitwise logical operations
- ❑ Shift - shift data in registers

Arithmetic operations

+ Addition

– Subtraction

*** Multiplication**

/ Division

Logical operations

\vee Logical OR

\wedge Logical AND

\oplus Logical Exclusive OR

\neg Not



Example Microoperations

- Add the content of R1 to the content of R2 and place the result in R1.

$$R1 \leftarrow R1 + R2$$

- Multiply the content of R1 by the content of R6 and place the result in PC.

$$PC \leftarrow R1 * R6$$

- Exclusive OR the content of R1 with the content of R2 and place the result in R1.

$$R1 \leftarrow R1 \oplus R2$$



Example Microoperations (Continued)

- Take the 1's Complement of the contents of R2 and place it in the PC.

$$PC \leftarrow \overline{R2}$$

- On condition K1 **OR** K2, the content of R1 is **Logic bitwise OR** with the content of R3 and the result placed in R1.

$$(K1 + K2): R1 \leftarrow R1 \vee R3$$

- NOTE: "+" (as in $K_1 + K_2$) and means "OR"
In $R1 \leftarrow R1 + R3$, + means "plus."

Control Expressions

- The **control expression** for an operation appears to the left of the operation and is separated from it by a colon
 - Control expressions specify the **logical condition** for the operation to occur
 - Control expression values of:
 - ▣ Logic "1" -- the operation occurs.
 - ▣ Logic "0" -- the operation is does not occur.
- Example:
 $\overline{X} K1 : R1 \leftarrow R1 + R2$
 $X K1 : R1 \leftarrow R1 + \overline{R2} + 1$
 - Variable K1 enables the add or subtract operation.
 - If $X = 0$, then $\overline{X} = 1$ so $\overline{X} K1 = 1$, activating the addition of R1 and R2.
 - If $X = 1$, then $X K1 = 1$, activating the addition of R1 and the two's complement of R2 (subtract).

Arithmetic Microoperations

- From Table 7-3:

Symbolic Designation	Description
$R0 \leftarrow R1 + R2$	Addition
$R0 \leftarrow \overline{R1}$	One's Complement
$R0 \leftarrow \overline{R1} + 1$	Two's Complement
$R0 \leftarrow R2 + \overline{R1} + 1$	R2 minus R1 (2's Comp)
$R1 \leftarrow R1 + 1$	Increment (count up)
$R1 \leftarrow R1 - 1$	Decrement (count down)

- Note that any register may be specified for source 1, source 2, or destination.
- These simple microoperations operate on the whole word

Logical Microoperations

- From Table 7-4:

Symbolic Designation	Description
$R0 \leftarrow \overline{R1}$	Bitwise NOT
$R0 \leftarrow R1 \vee R2$	Bitwise OR (sets bits)
$R0 \leftarrow R1 \wedge R2$	Bitwise AND (clears bits)
$R0 \leftarrow R1 \oplus R2$	Bitwise EXOR (complements bits)



Logical Microoperations (continued)

- Let $R1 = 10101010$,
and $R2 = 11110000$
- Then after the operation, $R0$ becomes:

R0	Operation
01010101	$R0 \leftarrow \overline{R1}$
11111010	$R0 \leftarrow R1 \vee R2$
10100000	$R0 \leftarrow R1 \wedge R2$
01011010	$R0 \leftarrow R1 \oplus R2$

Shift Microoperations

- From Table 7-5:
- Let $R2 = 11001001$
- Then after the operation, $R1$ becomes:

Symbolic Designation	Description
$R1 \leftarrow sl R2$	Shift Left
$R1 \leftarrow sr R2$	Shift Right

R1	Operation
10010010	$R1 \leftarrow sl R2$
01100100	$R1 \leftarrow sr R2$

- Note: These shifts "zero fill". Sometimes a separate flip-flop is used to provide the data shifted in, or to "catch" the data shifted out.
- Other shifts are possible (rotates, arithmetic) (see Chapter 10).



□ 谢 谢！