

Digital Logic Design

Chapter 6 – Digital Hardware Implementation

浙江大学计算机学院 王总辉

zhwang@zju.edu.cn

<http://course.zju.edu.cn>

2021年10月



Overview

- **The Design Space**

- Integrated Circuits
 - Levels of Integration
- CMOS Circuit Technology
 - CMOS Transistor Models
 - Circuits of Switches
 - Fully Complementary CMOS Circuits
 - Technology Parameters


- **Programming Technologies**

- ROMs
- PLAs
- PALs
- Lookup Tables


Integrated Circuits

- **Integrated circuit (informally, a “chip”) is a semiconductor crystal (most often silicon) containing the electronic components for the digital gates and storage elements which are interconnected on the chip.**
- **Terminology - Levels of chip integration**
 - ▣ *SSI (small-scale integrated)* - fewer than 10 gates
 - ▣ *MSI (medium-scale integrated)* - 10 to 100 gates
 - ▣ *LSI (large-scale integrated)* - 100 to thousands of gates
 - ▣ *VLSI (very large-scale integrated)* - thousands to 100s of millions of gates

MOS Transistor



 


MOS Transistor



 


Switch Models for MOS Transistors

   - **n-Channel – Normally Open (NO) Switch Contact**




   - **p-Channel – Normally Closed (NC) Switch Contact**




Circuits of Switch Models

- Series

 


- Parallel

 

Fully-Complementary CMOS Circuit

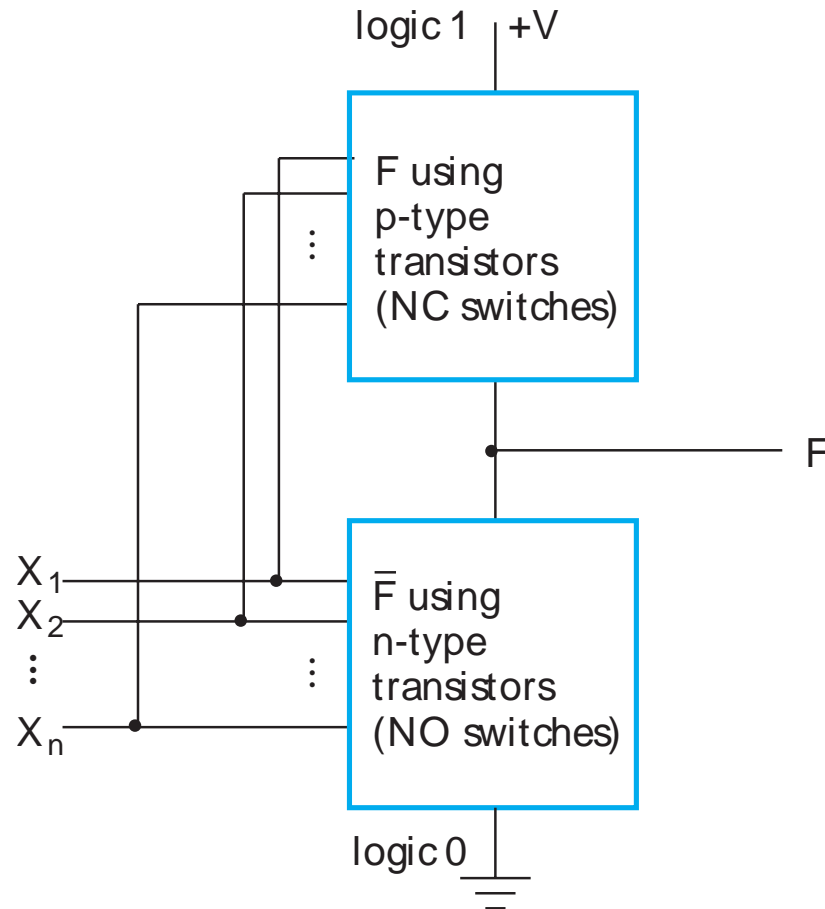- **Circuit structure for fully-complementary CMOS gate**



General Structure

CMOS Circuit Design Example


- Find a CMOS gate with the following function:

$$F = \bar{X} Z + \bar{Y} Z = (\bar{X} + \bar{Y})Z$$

- Beginning with F0, and using \bar{F}


$$\text{F0 Circuit: } \bar{F} = X Y + \bar{Z}$$

 - The switch model circuit in terms of NO switches:



CMOS Circuit Design Example

 - The switch model circuit for F1 in terms of NC contacts is the dual of the switch model circuit for F0:



- The function for this circuit is:

$$\text{F1 Circuit: } F = (\bar{X} + \bar{Y}) Z$$

which is the correct F.

Technology Parameters

- **Specific gate implementation technologies are characterized by the following parameters:**
 - ❑ *Fan-in* – the number of inputs available on a gate
 - ❑ *Fan-out* – the number of standard loads driven by a gate output
 - ❑ *Noise Margin* – the maximum external noise voltage superimposed on a normal input value that will not cause an undesirable change in the circuit output
 - ❑ *Cost for a gate* - a measure of the contribution by the gate to the cost of the integrated circuit
 - ❑ *Propagation Delay* – The time required for a change in the value of a signal to propagate from an input to an output
 - ❑ *Power Dissipation* – the amount of power drawn from the power supply and consumed by the gate



Fan-out

- **Fan-out can be defined in terms of a standard load**
 - Example: 1 standard load equals the load contributed by the input of 1 inverter.
 - *Transition time* -the time required for the gate output to change from H to L, t_{HL} , or from L to H, t_{LH}
 - The *maximum fan-out* that can be driven by a gate is the number of standard loads the gate can drive without exceeding its specified *maximum transition time*



Cost

- **In an integrated circuit:**
 - ❑ The cost of a gate is proportional to the chip area occupied by the gate
 - ❑ The gate area is roughly proportional to the number and size of the transistors and the amount of wiring connecting them
 - ❑ Ignoring the wiring area, the gate area is roughly proportional to the gate input count
 - ❑ So gate input count is a rough measure of gate cost
- **If the actual chip layout area occupied by the gate is known, it is a far more accurate measure**



Programming Technologies

- **Programming technologies are used to:**

- Control connections
- Build lookup tables
- Control transistor switching

- **The technologies**

- Control connections
 - Mask programming
 - Fuse
 - Antifuse
 - Single-bit storage element

Programming Technologies

- **The technologies (continued)**
 - Build lookup tables
 - Storage elements (as in a memory)
 - Transistor Switching Control
 - Stored charge on a floating transistor gate
 - Erasable
 - Electrically erasable
 - Flash (as in Flash Memory)
 - Storage elements (as in a memory)



Technology Characteristics


- **Permanent - Cannot be erased and reprogrammed**
 - Mask programming
 - Fuse
 - Antifuse
- **Reprogrammable**
 - Volatile - Programming lost if chip power lost
 - Single-bit storage element
 - Non-Volatile
 - Erasable
 - Electrically erasable
 - Flash (as in Flash Memory)




Programmable Configurations

- *Read Only Memory (**ROM**)* - a **fixed array of AND gates** and a **programmable array of OR gates**
- *Programmable Array Logic (**PAL**)⁰* - a **programmable array of AND gates** feeding a **fixed array of OR gates**.
- *Programmable Logic Array (**PLA**)* - a **programmable array of AND gates** feeding a **programmable array of OR gates**.
- *Complex Programmable Logic Device (**CPLD**) / Field-Programmable Gate Array (**FPGA**)* - complex enough to be called “architectures” - See VLSI Programmable Logic Devices reading supplement


ROM, PAL and PLA Configurations

 

(a) Programmable read-only memory (PROM)


 


 (b) Programmable array logic (PAL) device




(c) Programmable logic array (PLA) device

Logical symbols

  

AND Array

 

Read Only Memory

- Read Only Memories (**ROM**) or Programmable Read Only Memories (**PROM**) have:
 - N input lines,
 - M output lines, and
 - 2^N decoded minterms.
- **Fixed** AND array with 2^N outputs implementing all N-literal minterms.
- **Programmable** OR Array with M outputs lines to form up to M sum of minterm expressions.




Read Only Memory-2

- A program for a ROM or PROM is simply a multiple-output truth table
 - ▣ If a 1 entry, a connection is made to the corresponding minterm for the corresponding output
 - ▣ If a 0, no connection is made
- Can be viewed as a *memory* with the inputs as *addresses of data* (output values), hence ROM or PROM names!

The general structure of the read-only memory

The general structure of the ROM

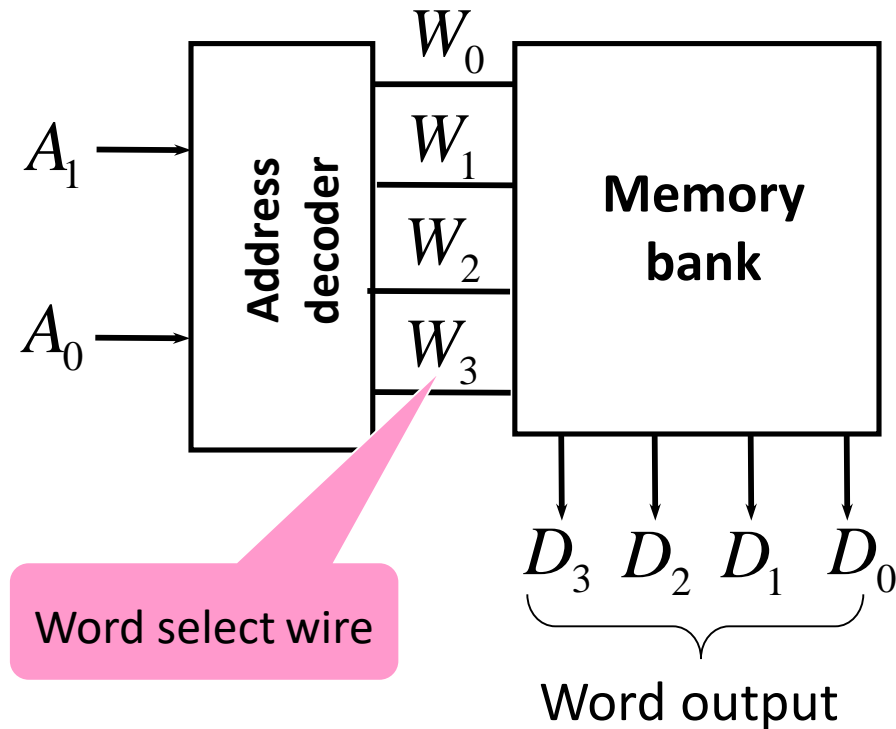
Size = $2^2 \times 4 \text{ bit} = 16 \text{ ROM}$
structure




The logical structure of the read-only memory

The **address decoder** is a completely minterms (Full decoder) circuit, that is a non-programmable, "AND" array

The memory bank is a "OR" array

 


A 4×4 ROM
specific circuit

 


"D0" bit wire "OR"
gate structure

Output information of ROM


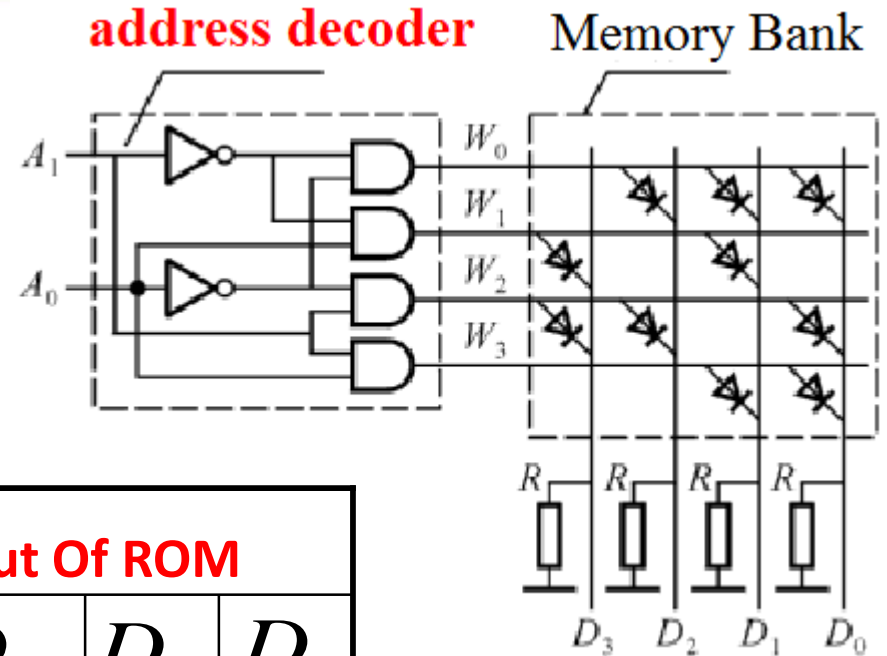


address		Word select wire	Output Of ROM			
A_1	A_0	W	D_3	D_2	D_1	D_0
<u>0</u>	<u>0</u>	W_0	<u>0</u>	<u>1</u>	<u>1</u>	<u>1</u>
<u>0</u>	<u>1</u>	W_1	<u>1</u>	<u>0</u>	<u>1</u>	<u>0</u>
<u>1</u>	<u>0</u>	W_2	<u>1</u>	<u>1</u>	<u>0</u>	<u>1</u>
<u>1</u>	<u>0</u>	W_3	<u>0</u>	<u>0</u>	<u>1</u>	<u>1</u>

ROM simplified logic symbol

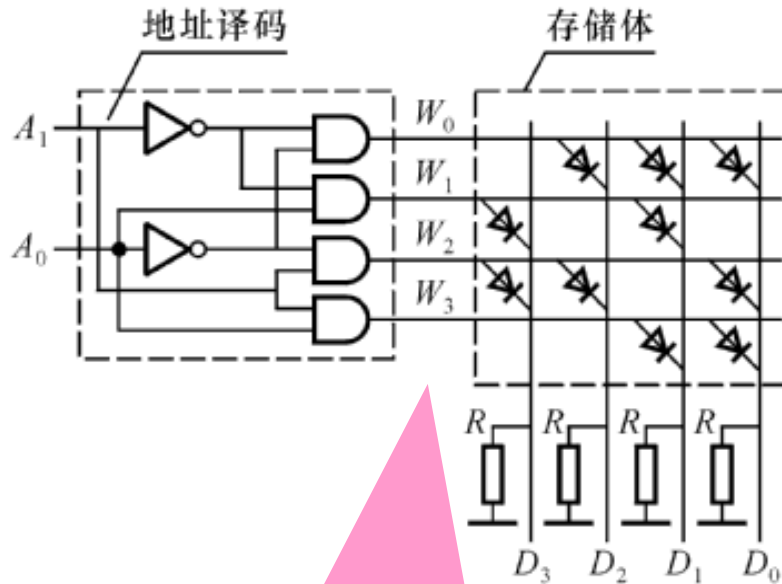


4 × 4ROM schematic

  

4 × 4ROM Simplified logic diagram

Read Only Memory Example

 - Example: A 8 X 4 ROM (N = 3 input lines, M= 4 output lines)
- The fixed "AND" array is a "decoder" with 3 inputs and 8 outputs implementing minterms.
- The programmable "OR" array uses a single line to represent all inputs to an OR gate. An "X" in the array corresponds to attaching the minterm to the OR
- Read Example: For input $(A_2, A_1, A_0) = 001$, output is $(F_3, F_2, F_1, F_0) = 0011$.
- What are functions F_3, F_2, F_1 and F_0 in terms of (A_2, A_1, A_0) ?





Programmable Array Logic (PAL)

- The PAL is the opposite of the ROM, having a **programmable** set of ANDs combined with **fixed** ORs.
- Disadvantage
 - ❑ ROM guaranteed to implement any M functions of N inputs. PAL may have too few inputs to the OR gates.
- Advantages
 - ❑ For given internal complexity, a PAL can have larger N and M
 - ❑ Some PALs have outputs that can be complemented, adding POS functions
 - ❑ No multilevel circuit implementations in ROM (without external connections from output to input). PAL has outputs from OR terms as internal inputs to all AND terms, making implementation of multi-level circuits easier.

Programmable Array Logic Example




- 4-input, 3-output PAL with fixed, 3-input OR terms
- What are the equations for F1 through F4?

$$F1 = \overline{A}\overline{B} + \overline{C}$$

$$F2 = \overline{A}B\overline{C} + AC + A\overline{B}$$

$$F3 =$$

$$F4 =$$

 



Programmable Logic Array (PLA)

- Compared to a ROM and a PAL, a PLA is the most flexible having a **programmable** set of ANDs combined with a **programmable** set of ORs.
- Advantages
 - ❑ A PLA can have large N and M permitting implementation of equations that are impractical for a ROM (because of the number of inputs, N, required)
 - ❑ A PLA has all of its product terms connectable to all outputs, overcoming the problem of the limited inputs to the PAL Ors
 - ❑ Some PLAs have outputs that can be complemented, adding POS functions



Programmable Logic Array (PLA)

- **Disadvantages**


- ❑ Often, the product term count limits the application of a PLA.
- ❑ Two-level multiple-output optimization is required to reduce the number of product terms in an implementation, helping to fit it into a PLA.
- ❑ Multi-level circuit capability available in PAL not available in PLA. PLA requires external connections to do multi-level circuits.

Programmable Logic Array Example


Use of the PLA to implement a set of functions:

- ❑ First, must be listed AND-Items of function (As much as possible many public items)
- ❑ Specifies whether need to be connected from the input to the AND gate array
- ❑ Specifies whether need to be connected from AND-array- output to the OR-array
- ❑ Whether the output is to be negated


		Inputs			Outputs	
					(T)	(C)
		A	B	C	F_1	F_2
$A\bar{B}$	1	1	0	—	1	—
AC	2	1	—	1	1	1
BC	3	—	1	1	—	1
$\bar{A}B\bar{C}$	4	0	1	0	1	—

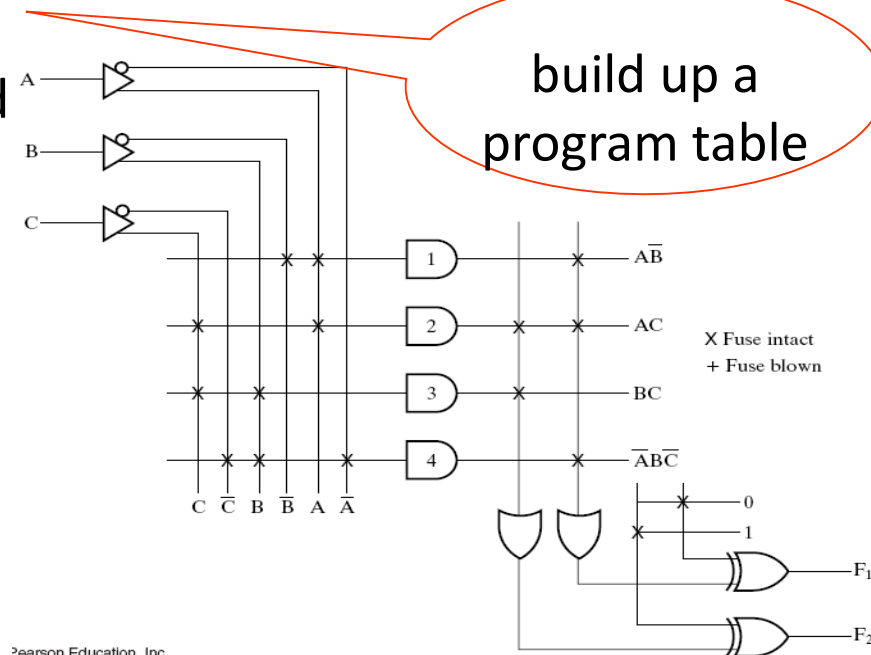

Generic array logic structure GAL

 

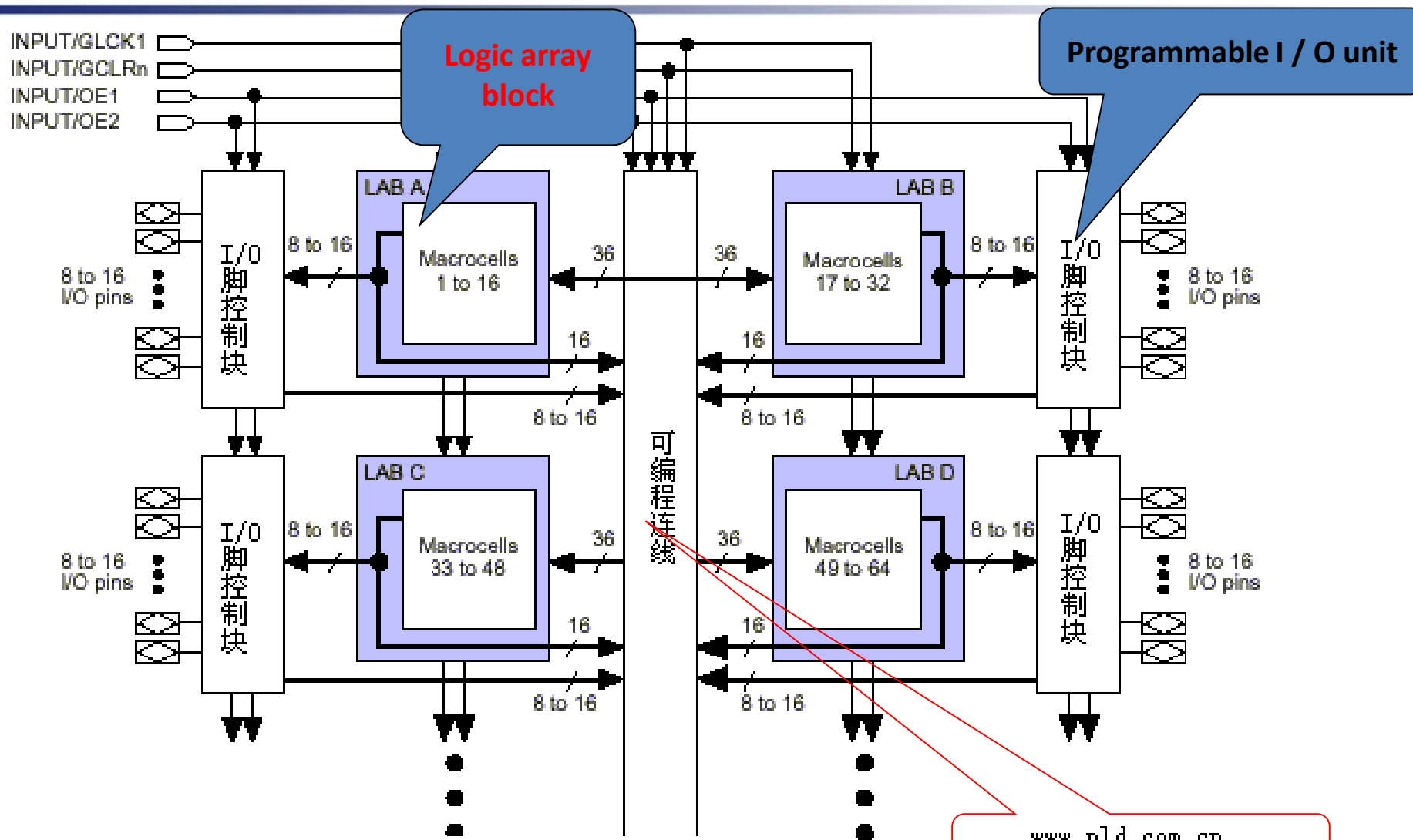Complex Programmable Logic Devices CPLD (Altera MAX7000S Series)




Programmable Gate Array: FPGA



- The internal structure is known as LCA (Logic Cell Array) is composed of three parts:

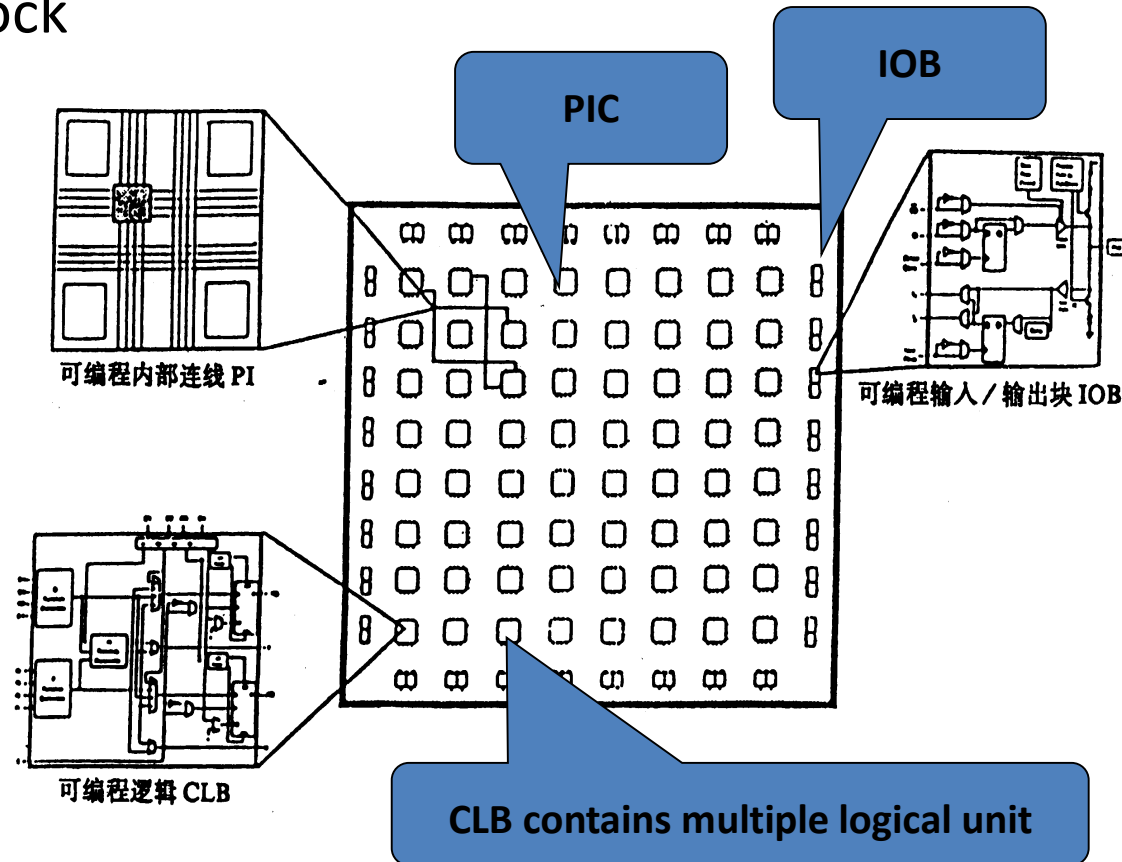
- ❑ Programmable logic block (CLB)
- ❑ Programmable input output module (IOB)
- ❑ Programmable internal connection (PIC)



- Is The Core of FPGA programmable universal logic function , composed of a RAM-based look-up table (LUT) may also be used as a memory.(480↑CLB, 24×20)



Switch array look-up table Principle

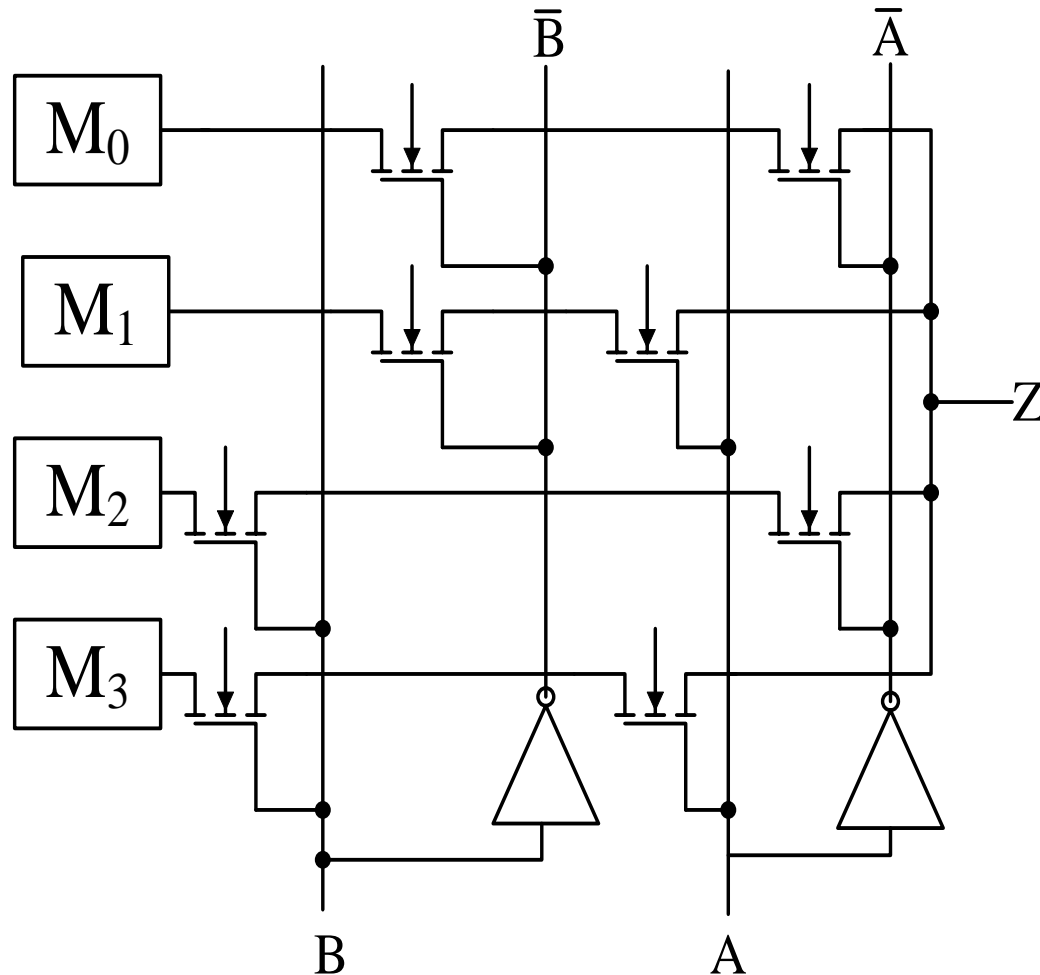

Configuration Table

Store	B	A	Z
M_0	0	0	M_0
M_1	0	1	M_1
M_2	1	0	M_2
M_3	1	1	M_3

Combinational Logic Implementation -ROM



- ROM is constituted by the variable decoder and OR gates
- function truth table is stored in the ROM
- Boolean function can be implemented in software

Inputs			Outputs						Decimal
A ₂	A ₁	A ₀	B ₅	B ₄	B ₃	B ₂	B ₁	B ₀	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

B₀=A₀


B₁="0"

ROM truth table

can select 8×4 bit ROM

Function input corresponding to the ROM address

 ROM output corresponding to the square value



ROM truth table

A ₂	A ₁	A ₀	B ₅	B ₄	B ₃	B ₂
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

How to choose the ROM?

Combinational Logic Implementation-PLAs



- Implement functions

$$F_1(A,B,C)$$

$$=\Sigma m(0,1,2,4)$$

$$F_2(A,B,C)$$

$$=\Sigma m(0,5,6,7)$$

- Use of K-map

simplification

- How the entries at least (shared)?

- Completion of the programming table

		B			
		BC		11	10
A	0	1	1	0	1
	1	1	0	0	0

$$F_1 = \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{B}\overline{C}$$

$$\overline{F}_1 = AB + AC + BC$$


		B			
		BC		11	10
A	0	1	0	0	0
	1	0	1	1	1

$$F_2 = AB + AC + \overline{A}\overline{B}\overline{C}$$

$$\overline{F}_2 = \overline{A}\overline{C} + \overline{A}\overline{B} + \overline{A}\overline{B}\overline{C}$$

PLA programming table

	Product term	Outputs				
		Inputs (C)			(T)	
		A	B	C	F ₁	F ₂
AB	1	1	1	—	1	1
AC	2	1	—	1	1	1
BC	3	—	1	1	1	—
$\overline{A}\overline{B}\overline{C}$	4	0	0	0	—	1

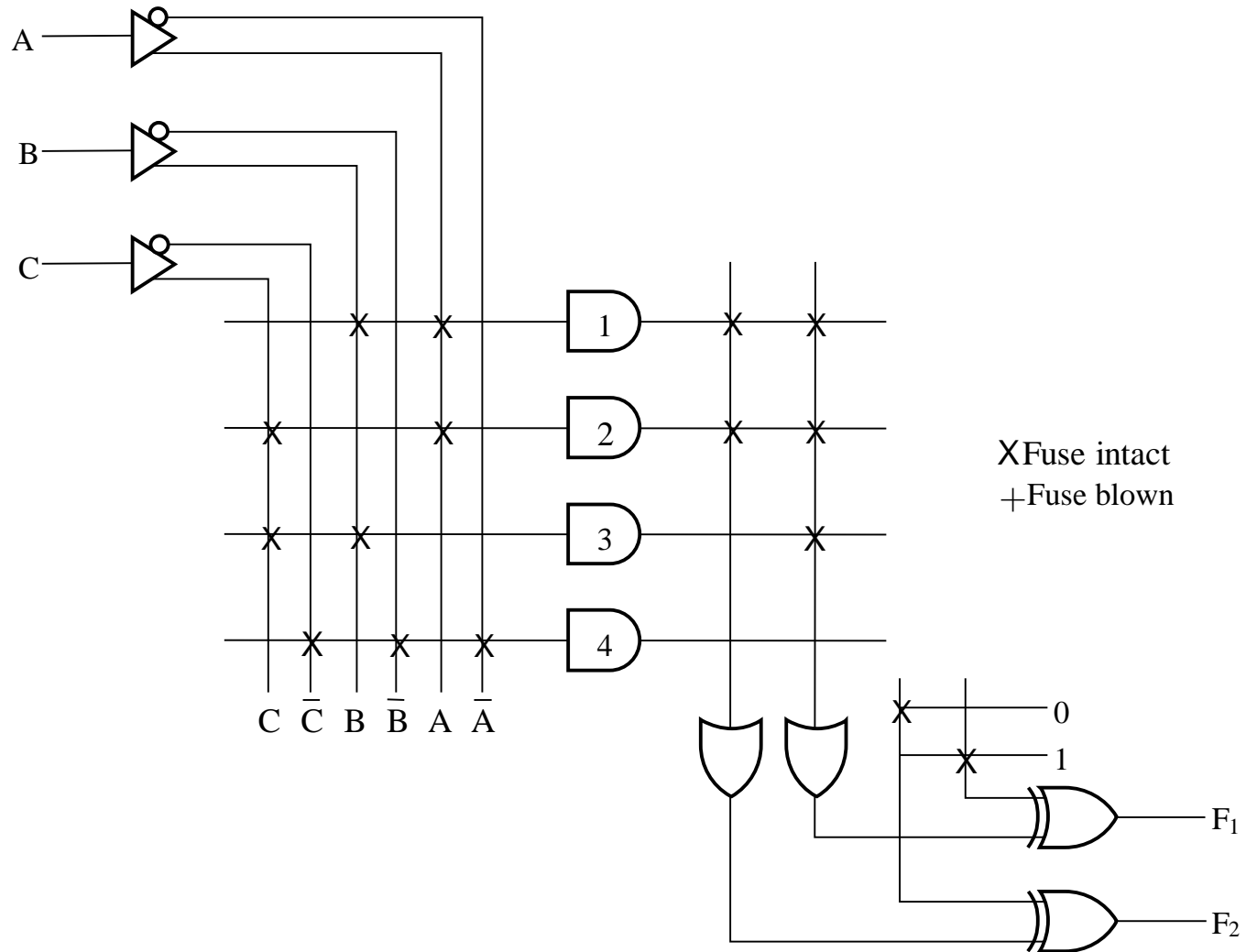



- Implement functions :

$$W(A,B,C,D)=\Sigma m(1,12,13)$$

$$X(A,B,C,D)=\Sigma m(7,8,9,10,11,12,13,14,15)$$

$$Y(A,B,C,D)=\Sigma m(0,2,3,4,5,6,7,8,9,10,11,15)$$

$$Z(A,B,C,D)=\Sigma m(1,2,8,12,13)$$

simplification follows :

$$W=ABC\bar{D}+\bar{A}\bar{B}C\bar{D}$$


$$X=A+BCD$$

$$Y=\bar{A}B+CD+\bar{B}\bar{D}$$

$$\begin{aligned} Z &= ABC\bar{D}+\bar{A}\bar{B}C\bar{D}+A\bar{C}\bar{D}+\bar{A}\bar{B}C\bar{D} \\ &= \mathbf{W}+A\bar{C}\bar{D}+\bar{A}\bar{B}C\bar{D} \end{aligned}$$

PAL Implement connection

Product term	AND Inputs					Outputs
	A	B	C	D	W	
1	1	1	0	—	—	$W = ABC\bar{C}$ $+ \bar{A}\bar{B}C\bar{D}$
2	0	0	1	0	—	
3	—	—	—	—	—	
4	1	—	—	—	—	$X = A$ $+ BCD$
5	—	1	1	1	—	
6	—	—	—	—	—	
7	0	1	—	—	—	$Y = \bar{A}B$ $+ CD$ $+ \bar{B}\bar{D}$
8	—	—	1	1	—	
9	—	0	—	0	—	
10	—	—	—	—	1	$Z = W$ $+ A\bar{C}\bar{D}$ $+ \bar{A}\bar{B}C\bar{D}$
11	1	—	0	0	—	
12	0	0	0	1	—	

 



Thank You !