



# Digital Logic Design

## Chapter 3 – Combinational Logic Design Implementation Technology and Logic Design

浙江大学计算机学院 王总辉

zhwang@zju.edu.cn

<http://course.zju.edu.cn>

2023年10月

---



# Overview

---

- **Part 1 – Design Procedure**

- Steps

- Specification
    - Formulation
    - Optimization
    - Technology Mapping

- Beginning Hierarchical Design

- Technology Mapping - AND, OR, and NOT to NAND or NOR

- Verification

- Manual
    - Simulation

# Overview (continued)

---

## ● Part 2 – Combinational Logic

- Functions and functional blocks
- Rudimentary logic functions
- Decoding using Decoders
  - Implementing Combinational Functions with Decoders
- Encoding using Encoders
- Selecting using Multiplexers
  - Implementing Combinational Functions with Multiplexers

# learning demands:



- Understanding the characteristics of combinational logic circuits
- **Skilled to master** the basic method of combination circuit analysis and design of the basic method
- Understanding gate properties and main technological parameters
- Understanding the programmable chip structure Mastered programmable implement technology

# Combinational Circuits



- **Logic Circuits**


major categories {  
Combinational Logic Circuits  
Sequential Logic Circuits

Combinational circuit is defined:

--If a stable **output value** of logic circuit, at any given moment, the value **depends only** on set of the **input values** of **the moment**, **regardless** of the **past input** value, then the circuit is a combinational logic circuit.
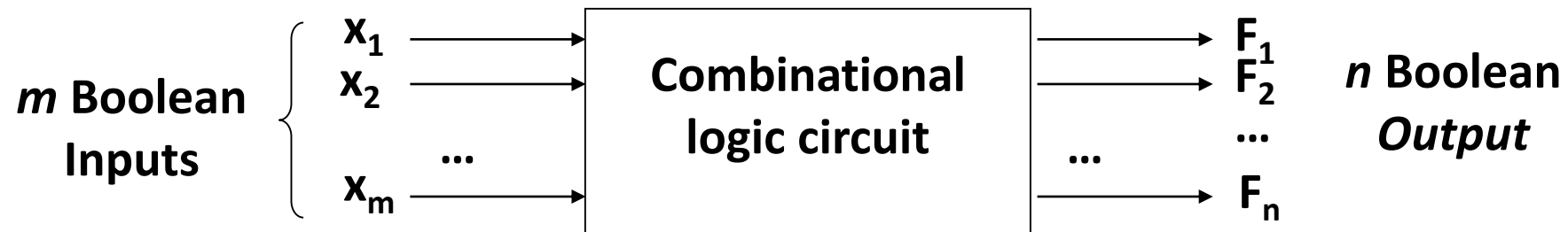
# Combinational circuit characteristics

- **A combinational logic circuit has:**
  - A set of  $m$  Boolean inputs,
  - A set of  $n$  Boolean outputs, and
  - $n$  switching functions, each mapping the  $2^m$  input combinations to an output such that the current output depends only on the current input values
- **A block diagram:**



$$F_i = f_i(x_1, x_2, \dots, x_m), \quad i=1, 2, \dots, n$$

( **without any memory element and feedback loop.**  
**input signal unidirectional transmission** )

# Combinational circuit analysis method



## 1. To write logic function according to circuit

- From input to the output, level by level, to write expression of each door
- Then, write a logical expression of the entire circuit, according to the logical relationship among each door
- simplifying function expression

## 2. Lists the truth table

- analyzing the variables causal relationship and logic functions between input and output

## 3. Event functional analysis

- assigning variable to the actual meaning, sum actual functionality up the circuit
- To draw logic waveform diagram of input and output

## 4. Evaluation or improvement

- Evaluate of the design rationality

# Analyzes circuits logic functions



List the expression level by level

$$P_1 = A \oplus B$$

$$P_2 = B \oplus C$$


$$P_3 = \overline{\overline{A} + \overline{B}} = AB$$

$$P_4 = \overline{A + C}$$

$$P_5 = \overline{P_1 P_2} = \overline{(A \oplus B) \cdot (B \oplus C)}$$

$$P_6 = P_3 + P_4 = AB + \overline{A + C}$$
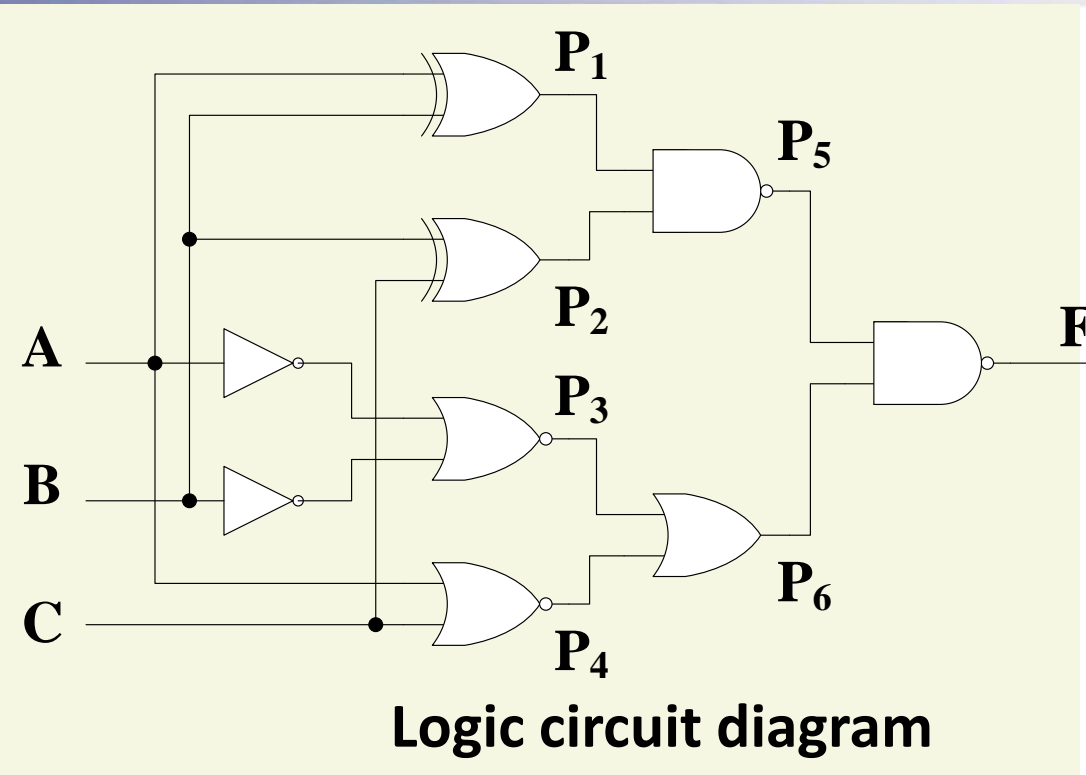
$$F = \overline{P_5 \cdot P_6} = \overline{\overline{(A \oplus B) \cdot (B \oplus C)} \cdot (AB + \overline{A + C})}$$





# simplifying function expression

$$\begin{aligned}
 F &= (A \oplus B)(B \oplus C) + \overline{AB} + \overline{A + C} \\
 &= (A\bar{B} + \bar{A}B)(B\bar{C} + \bar{B}C) + (\bar{A} + \bar{B})(A + C) \\
 &= A\bar{B}C + \bar{A}B\bar{C} + \bar{A}C + A\bar{B} + \bar{B}C \\
 &= \bar{A}B\bar{C} + \bar{A}C + A\bar{B} + \bar{B}C \\
 &= \bar{A}C + A\bar{B} + \bar{A}B\bar{C} \\
 &= \bar{A}(C + B\bar{C}) + A\bar{B} \\
 &= \bar{A}C + \bar{A}B + A\bar{B} \\
 &= \bar{A}C + (A \oplus B)
 \end{aligned}$$

Lists the truth table

| A | B | C | $A \oplus B$ | $\bar{A}C$ | F |
|---|---|---|--------------|------------|---|
| 0 | 0 | 0 | 0            | 0          | 0 |
| 0 | 0 | 1 | 0            | 1          | 1 |
| 0 | 1 | 0 | 1            | 0          | 1 |
| 0 | 1 | 1 | 1            | 1          | 1 |
| 1 | 0 | 0 | 1            | 0          | 1 |
| 1 | 0 | 1 | 1            | 0          | 1 |
| 1 | 1 | 0 | 0            | 0          | 0 |
| 1 | 1 | 1 | 0            | 0          | 0 |

# simplifying function expression

$$\begin{aligned}
 F &= (A \oplus B) + C \\
 &= (A \oplus B) + C \\
 &= A\bar{B} + \bar{A}B + C \\
 &= \bar{A}B\bar{C} + \bar{A}C + A\bar{B} + \bar{B}C
 \end{aligned}$$

## Functional Analysis :

Seen from the truth table,  $F = 1$ , the condition is  $A \neq B$ , or  $B < C$ , **it's a condition determination circuit**


## Evaluation:

The original design is not the best, replaced by the following simplest circuit:

$$F = \bar{A}C + (A \oplus B)$$

## Lists the truth table

| A | B | C | $A \oplus B$ | $\bar{A}C$ | F |
|---|---|---|--------------|------------|---|
| 0 | 0 | 0 | 0            | 0          | 0 |
| 0 | 0 | 1 | 0            | 1          | 1 |
| 0 | 1 | 0 | 1            | 0          | 1 |
| 0 | 1 | 1 | 1            | 0          | 1 |
| 1 | 0 | 0 | 1            | 0          | 1 |
| 1 | 0 | 1 | 1            | 0          | 1 |
| 1 | 1 | 0 | 0            | 0          | 0 |
| 1 | 1 | 1 | 0            | 0          | 0 |

 

# Design Procedure

## 1. Specification (**Logical abstraction**)

- ❑ Write a specification for the circuit if one is not already available

## 2. Formulation(**Logical abstraction to write logic expression**)

- ❑ Derive a truth table or initial Boolean equations that define the required relationships between the inputs and outputs, if not in the specification
- ❑ Apply hierarchical design if appropriate

# Design Procedure (continued)

## 3. Optimization(**The simplification** )

- ❑ Apply 2-level and multiple-level optimization
- ❑ Draw a logic diagram or provide a netlist for the resulting circuit using ANDs, ORs, and inverters

## 4. Technology Mapping(**Converted into the suitable expression**)

- ❑ Map the logic diagram or net-list to the implementation technology selected

## 5. Verification

- ❑ Verify the correctness of the final design manually or using simulation

## 1. Logical abstraction

- 1) Analyzes Causality of events, Determine:  
Input variables --Independent variables  
Output variable -- Function
- 2) Defining meaning of the logical variables (state):  
assigning values to variables
- 3) Lists the Truth table according to the Causality


## 2. To write logic expression (Minterm)

## 3. The simplification—K-map

## 4. Technology Mapping

Converted into the suitable expression, and draw the logical connection diagram
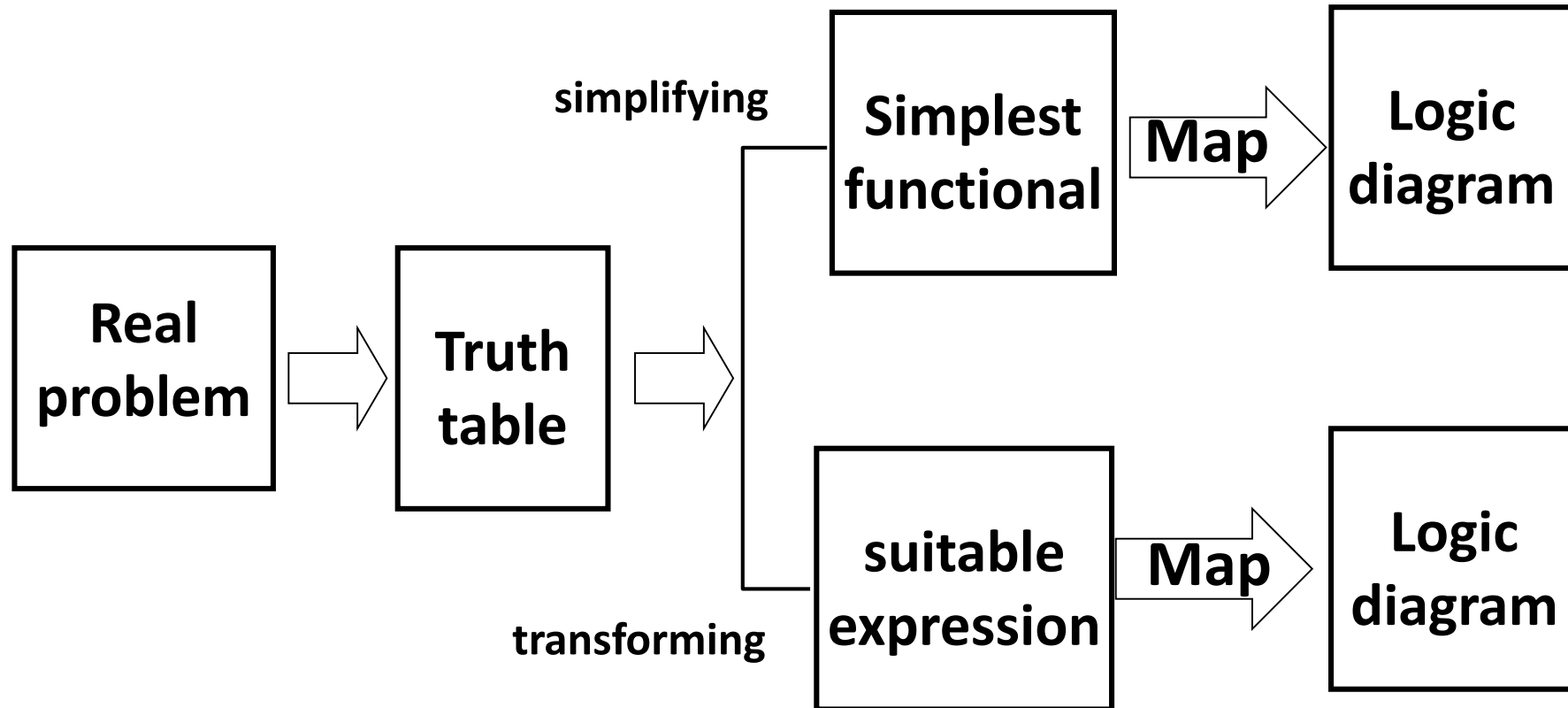
## 5. Designing circuit module with HDL description



# Design Example 1

Only one lamp in the dormitory, but there are three beds. Now at the side of each bed install a switch that can independently control the light. Please design this circuit with the least gates.

## Step 1: Logical abstraction

Analyzes Causality :

Switch as Input variables :  $S_1$ 、 $S_2$ 、 $S_3$

Control the light as Output variable:  $F$

Assigning Switch : Pressed is "1", pounce to "0"

Assigning Output: Brighten is "1", dimmed to "0"

## Step 2: Derive logic expression

$$F = \bar{S}_3 \bar{S}_2 S_1 + \bar{S}_3 S_2 \bar{S}_1 + S_3 \bar{S}_2 \bar{S}_1 + S_3 S_2 S_1$$

Truth table

| $S_3$ | $S_2$ | $S_1$ | $F$ |
|-------|-------|-------|-----|
| 0     | 0     | 0     | 0   |
| 0     | 0     | 1     | 1   |
| 0     | 1     | 0     | 1   |
| 0     | 1     | 1     | 0   |
| 1     | 0     | 0     | 1   |
| 1     | 0     | 1     | 0   |
| 1     | 1     | 0     | 0   |
| 1     | 1     | 1     | 1   |

# Design Example

$$F = \bar{S}_3 \bar{S}_2 S_1 + \bar{S}_3 S_2 \bar{S}_1 + S_3 \bar{S}_2 \bar{S}_1 + S_3 S_2 S_1$$

| $S_3$ | $S_2$ | $S_1$ | F |
|-------|-------|-------|---|
| 0     | 0     | 0     | 0 |
| 0     | 0     | 1     | 1 |
| 0     | 1     | 0     | 1 |
| 0     | 1     | 1     | 0 |
| 1     | 0     | 0     | 1 |
| 1     | 0     | 1     | 0 |
| 1     | 1     | 0     | 0 |
| 1     | 1     | 1     | 1 |


Step 3: simplifying

| $S_3 \backslash S_2 S_1$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0                        |    | 1  |    | 1  |
| 1                        | 1  |    | 1  |    |

Has been the most simple



## Step 4: Logical connection diagram

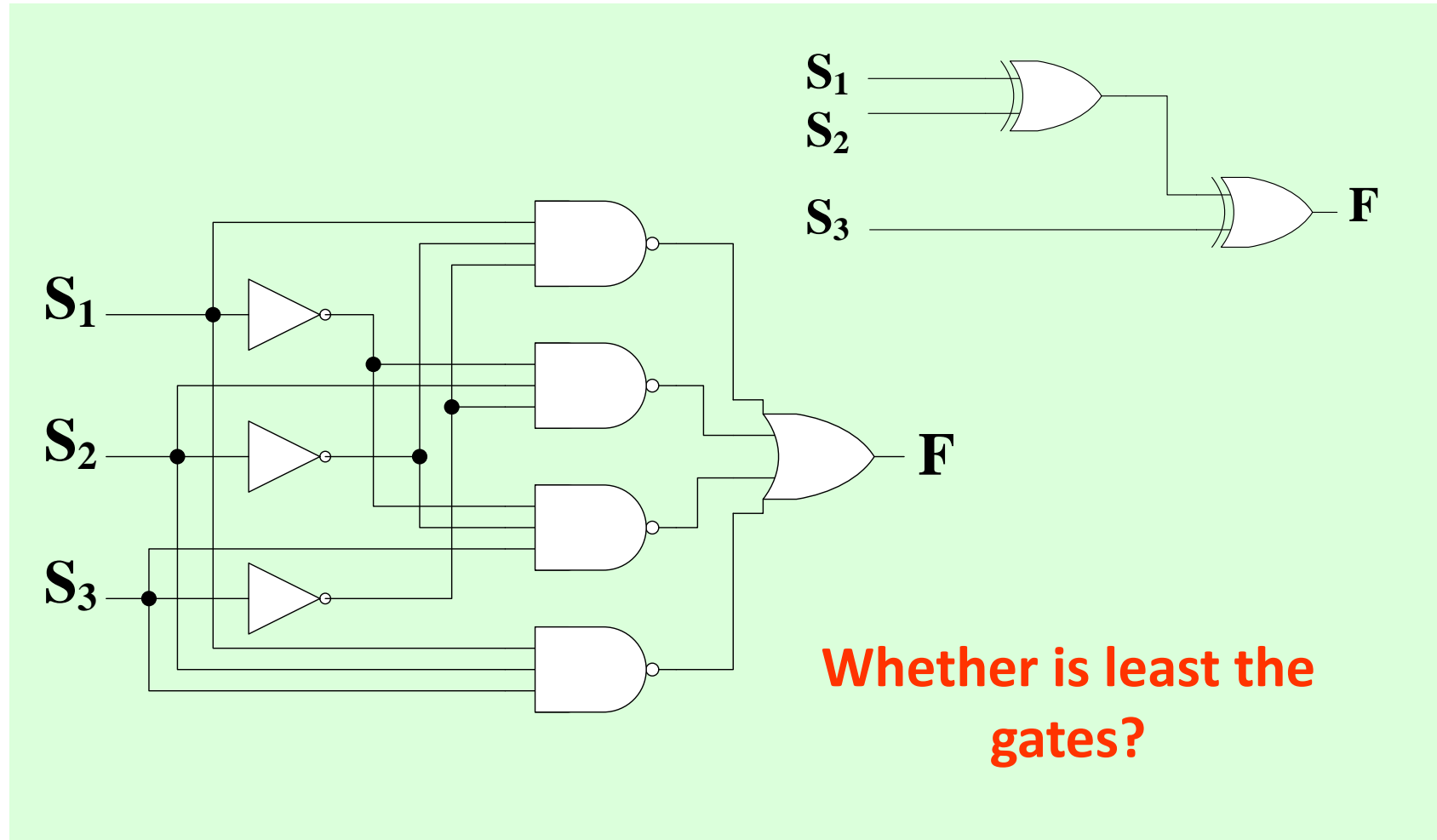

## Step 5: Designing circuit module with HDL description

$$F = \bar{S}_3 \bar{S}_2 S_1 + \bar{S}_3 S_2 \bar{S}_1 + S_3 \bar{S}_2 \bar{S}_1 + S_3 S_2 S_1$$

```
module lamp_control(s1,s2,s3,F );  
    input  s1,s2,s3;  
    output F;  
    wire  s1,s2,s3,f;  
  
    assign F= (~s3&~s2&s1) | (~s3&s2&~s1) | (s3&s2&s1) ;  
  
endmouule
```

# Beginning Hierarchical Design

- **To control the complexity of the function mapping inputs to outputs:**
  - ❑ Decompose the function into smaller pieces called *blocks*
  - ❑ Decompose each block's function into smaller blocks, repeating as necessary until all blocks are small enough
  - ❑ Any block not decomposed is called a *primitive block*
  - ❑ The collection of all blocks including the decomposed ones is a *hierarchy*

## Module definition

```
module lamp_control(s1,s2,s3,F );
```

```
    input  s1,s2,s3;
```


```
    output F;
```

- **Example: 9-input parity tree (see next slide)**


# Hierarchy for Parity Tree Example




**Top Level: 9 inputs, one output**

 

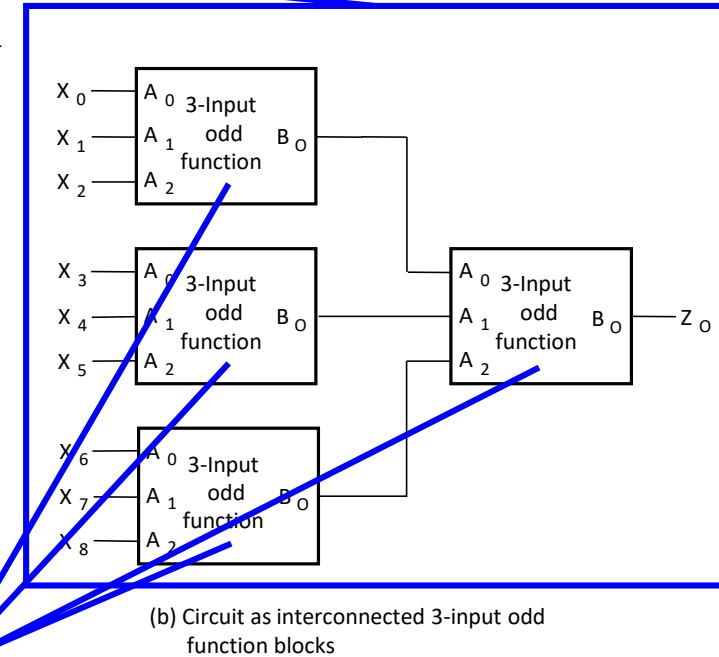
**2nd Level: Four 3-bit odd parity trees in two levels**



 **3rd Level: Two 2-bit exclusive-OR functions**



**Primitives: Four 2-input NAND gates**

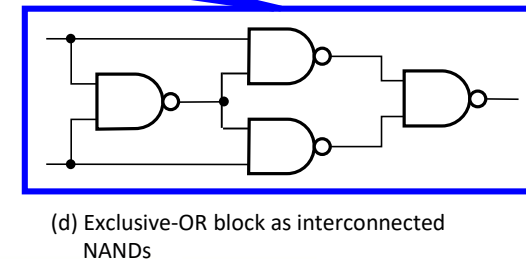

**Design requires  $4 \times 2 \times 4 = 32$  2-input NAND gates**



# Reusable Functions

---

- Whenever possible, we try to decompose a complex design into common, *reusable* function blocks
- These blocks are
  - verified and well-documented
  - placed in libraries for future use



# Top-Down versus Bottom-Up

---

- A **top-down design** proceeds from an abstract, high-level specification to a more and more detailed design by decomposition and successive refinement ***What do we build?***
- A **bottom-up design** starts with detailed primitive blocks and combines them into larger and more complex functional blocks ***What we use to build?***
- Design usually proceeds **top-down** to known building blocks ranging from **complete** CPUs **to primitive** logic gates or electronic components.
- Much of the material in this chapter is devoted to learning about combinational blocks used in top-down design.

# Design Example 2

## 1. Specification

- ❑ BCD to Excess-3 code converter
- ❑ Transforms BCD code for the decimal digits to Excess-3 code for the decimal digits
- ❑ BCD code words for digits 0 through 9: 4-bit patterns 0000 to 1001, respectively
- ❑ Excess-3 code words for digits 0 through 9: 4-bit patterns consisting of 3 (binary 0011) added to each BCD code word
- ❑ Implementation:
  - multiple-level circuit
  - NAND gates (including inverters)

# Design Example (continued)

## 2. Formulation

- Conversion of 4-bit codes can be most easily formulated by a truth table

- Variables

- BCD:

- A,B,C,D

- Variables

- Excess-3

- W,X,Y,Z

- Don't Cares

- BCD 1010

- to 1111

| Input BCD<br>A B C D | Output Excess-3<br>W X Y Z |
|----------------------|----------------------------|
| 0 0 0 0              | 0 0 1 1                    |
| 0 0 0 1              | 0 1 0 0                    |
| 0 0 1 0              | 0 1 0 1                    |
| 0 0 1 1              | 0 1 1 0                    |
| 0 1 0 0              | 0 1 1 1                    |
| 0 1 0 1              | 1 0 0 0                    |
| 0 1 1 0              | 1 0 0 1                    |
| 0 1 1 1              | 1 0 1 0                    |
| 1 0 0 0              | 1 0 1 1                    |
| 1 0 0 1              | 1 0 1 1                    |

1100



# Design Example (continued)

## 3. Optimization





- a. 2-level using K-maps

$$W = A + BC + BD$$

$$X = \overline{B}C + \overline{B}D + B\overline{C}\overline{D}$$

$$Y = CD + \overline{C}\overline{D}$$

$$Z = \overline{D}$$

    

# Design Example (continued)

## 3. Optimization (continued)

b. Multiple-level using transformations

$$W = A + BC + BD$$

$$X = \overline{B}C + \overline{B}D + B\overline{C}\overline{D}$$

$$Y = CD + \overline{C}\overline{D}$$

$$Z = \overline{D} \quad G = 7 + 10 + 6 + 0 = 23$$

□ Perform extraction, finding factor:  $T_1 = C + D$

$$T_1 = C + D$$

$$W = A + BT_1$$

$$X = \overline{B}T_1 + B\overline{C}\overline{D}$$

$$Y = CD + \overline{C}\overline{D}$$

$$Z = \overline{D}$$

# Design Example (continued)

## 3. Optimization (continued)

- b. Multiple-level using transformations

$$\mathbf{T}_1 = \mathbf{C} + \mathbf{D}$$

$$\mathbf{W} = \mathbf{A} + \mathbf{B}\mathbf{T}_1$$

$$\mathbf{X} = \overline{\mathbf{B}}\mathbf{T}_1 + \mathbf{B}\overline{\mathbf{C}}\overline{\mathbf{D}}$$

$$\mathbf{Y} = \mathbf{C}\mathbf{D} + \overline{\mathbf{C}}\overline{\mathbf{D}}$$

$$\mathbf{Z} = \overline{\mathbf{D}}$$

$$\mathbf{G} = 2+4+7+6+0=19$$

- An additional extraction not shown in the text since it uses a Boolean transformation:

$$\overline{\mathbf{T}}_1 = \overline{\mathbf{C} + \mathbf{D}} = \overline{\mathbf{C}}\overline{\mathbf{D}}$$

$$\mathbf{W} = \mathbf{A} + \mathbf{B}\mathbf{T}_1$$

$$\mathbf{X} = \overline{\mathbf{B}}\mathbf{T}_1 + \mathbf{B}\overline{\mathbf{T}}_1$$

$$\mathbf{Y} = \mathbf{C}\mathbf{D} + \overline{\mathbf{T}}_1$$



$$\mathbf{Z} = \overline{\mathbf{D}}$$

$$\mathbf{G} = 2 + 1 + 4 + 6 + 4 + 0 = 17!$$

# Design Example (continued)
  
## 4. Technology Mapping

- Mapping with a library containing inverters and 2-input NAND, 2-input NOR, and 2-2 AOI gates



## 5. Hardware Description module design

```
module BCD_ Excess_3( A,B,C,D,W,X,Y,Z );  
    input  A,B,C,D;  
    output W,X,Y,Z;  
    wire A,B,C,D , W,X,Y,Z,T1;  
  
    assign T1= C|D;  
    assign W= A|B&C|B&D ;  
    assign X = ~B&T1|B&(~C&~D);  
    assign Y = C&D|~C&~D;  
    assign Z= ~D ;  
  
endmodule
```



# Technology Mapping

---

- **Mapping Procedures**

- To NAND gates
- To NOR gates
- Mapping to multiple types of logic blocks is covered in the reading supplement: Advanced Technology Mapping.



# Mapping to NAND gates

---

- **Assumptions:**


- Gate loading and delay are ignored
- Cell library contains an inverter and  $n$ -input NAND gates,  $n = 2, 3, \dots$
- An AND, OR, inverter schematic for the circuit is available

- **The mapping is accomplished by:**

- Replacing AND and OR symbols,
- Pushing inverters through circuit fan-out points, and
- Canceling inverter pairs


# NAND Mapping Algorithm

## 1. Replace ANDs and ORs:

 

 
## 2. Repeat the following pair of actions until there is at most one inverter between :

- A circuit input or driving NAND gate output, and
- The attached NAND gate inputs.







# NAND Mapping Example

 


(a)

 

(b)

 

(c)

 

(d)


# Mapping to NOR gates

---

- **Assumptions:**
  - Gate loading and delay are ignored
  - Cell library contains an inverter and  $n$ -input NOR gates,  $n = 2, 3, \dots$
  - An AND, OR, inverter schematic for the circuit is available
- **The mapping is accomplished by:**
  - Replacing AND and OR symbols,
  - Pushing inverters through circuit fan-out points, and
  - Canceling inverter pairs


# NOR Mapping Algorithm

## 1. Replace ANDs and ORs:

 

 
## 2. Repeat the following pair of actions until there is at most one inverter between :

- A circuit input or driving NAND gate output, and
- The attached NAND gate inputs.



# NOR Mapping Example

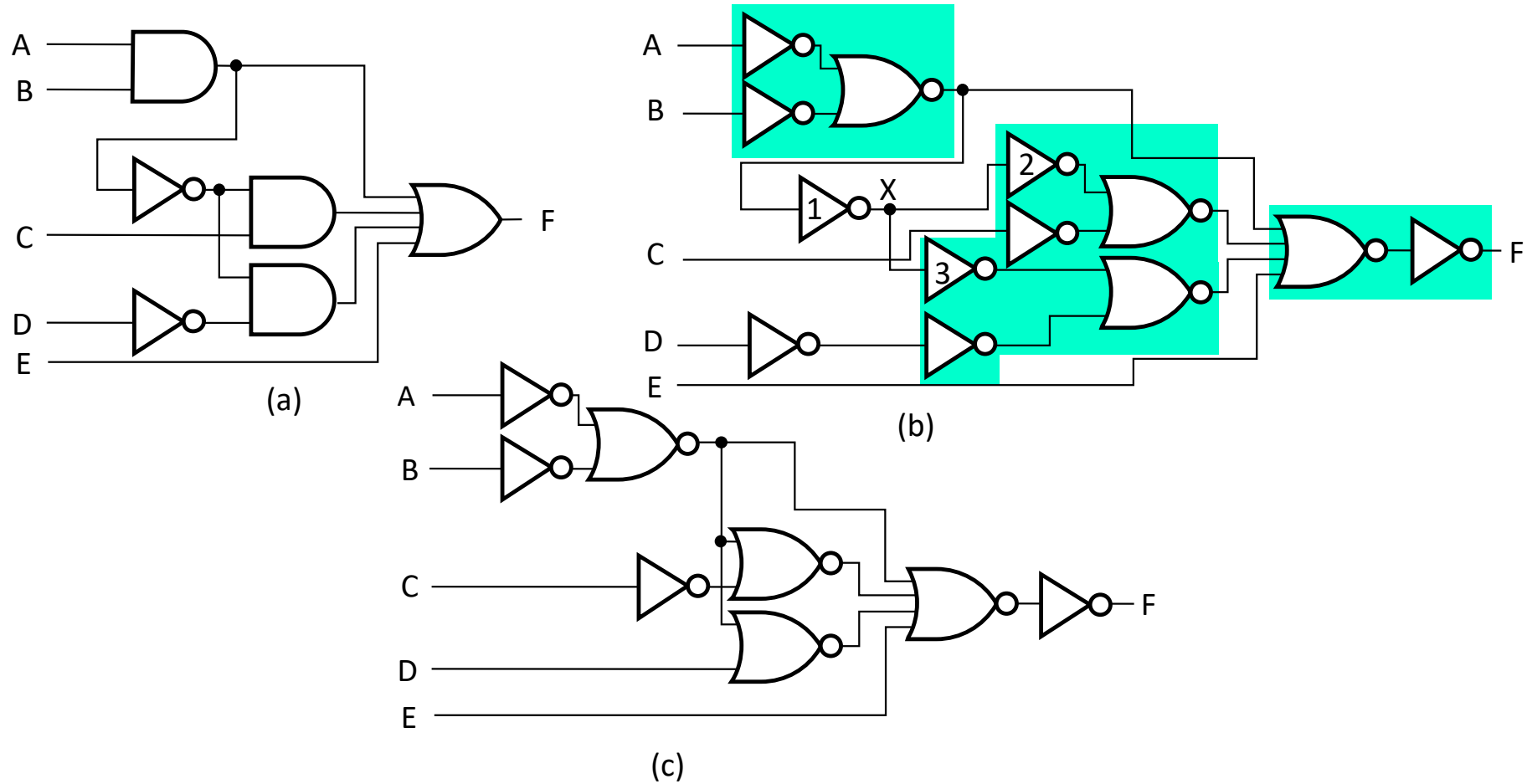



# Verification

---

- **Verification - show that the final circuit designed implements the original specification**
- **Simple specifications are:**
  - ❑ truth tables
  - ❑ Boolean equations
  - ❑ HDL code
- **If the above result from formulation and are not the original specification, it is critical that the formulation process be flawless for the verification to be valid!**



# Basic Verification Methods

---

## ● Manual Logic Analysis

- ❑ Find the truth table or Boolean equations for the final circuit
- ❑ Compare the final circuit truth table with the specified truth table, or
- ❑ Show that the Boolean equations for the final circuit are equal to the specified Boolean equations

## ● Simulation

- ❑ Simulate the final circuit (or its netlist, possibly written as an HDL) and the specified truth table, equations, or HDL description using test input values that fully validate correctness.
- ❑ The obvious test for a combinational circuit is application of all possible “care” input combinations from the specification

# Verification Example: Manual Analysis



- **BCD-to-Excess 3 Code Converter**

- Find the SOP Boolean equations from the final circuit.
- Find the truth table from these equations
- Compare to the formulation truth table

- **Finding the Boolean Equations:**

$$T_1 = \overline{\overline{C + D}} = C + D$$

$$W = \overline{\overline{A(T_1 B)}} = A + BT_1$$

$$X = \overline{\overline{(T_1 B)(\overline{BCD})}} = \overline{BT_1} + \overline{BCD}$$

$$Y = \overline{CD} + \overline{\overline{CD}} = \overline{CD} + CD$$

$$Z = \overline{D}$$

# Verification Example: Manual Analysis



- Find the circuit truth table from the equations and compare to specification truth table:

| Input BCD<br>A B C D | Output Excess -3<br>WXYZ |
|----------------------|--------------------------|
| 0 0 0 0              | 0 0 1 1                  |
| 0 0 0 1              | 0 1 0 0                  |
| 0 0 1 0              | 0 1 0 1                  |
| 0 0 1 1              | 0 1 1 0                  |
| 0 1 0 0              | 0 1 1 1                  |
| 0 1 0 1              | 1 0 0 0                  |
| 0 1 1 0              | 1 0 0 1                  |
| 0 1 1 1              | 1 0 1 0                  |
| 1 0 0 0              | 1 0 1 1                  |
| 1 0 0 1              | 1 0 1 1                  |

The tables match!




- **Simulation procedure:**

- Use a schematic editor or text editor to enter a gate level representation of the final circuit
- Use a waveform editor or text editor to enter a test consisting of a sequence of input combinations to be applied to the circuit
  - This test should guarantee the correctness of the circuit if the simulated responses to it are correct
  - Short of applying all possible “care” input combinations, generation of such a test can be difficult
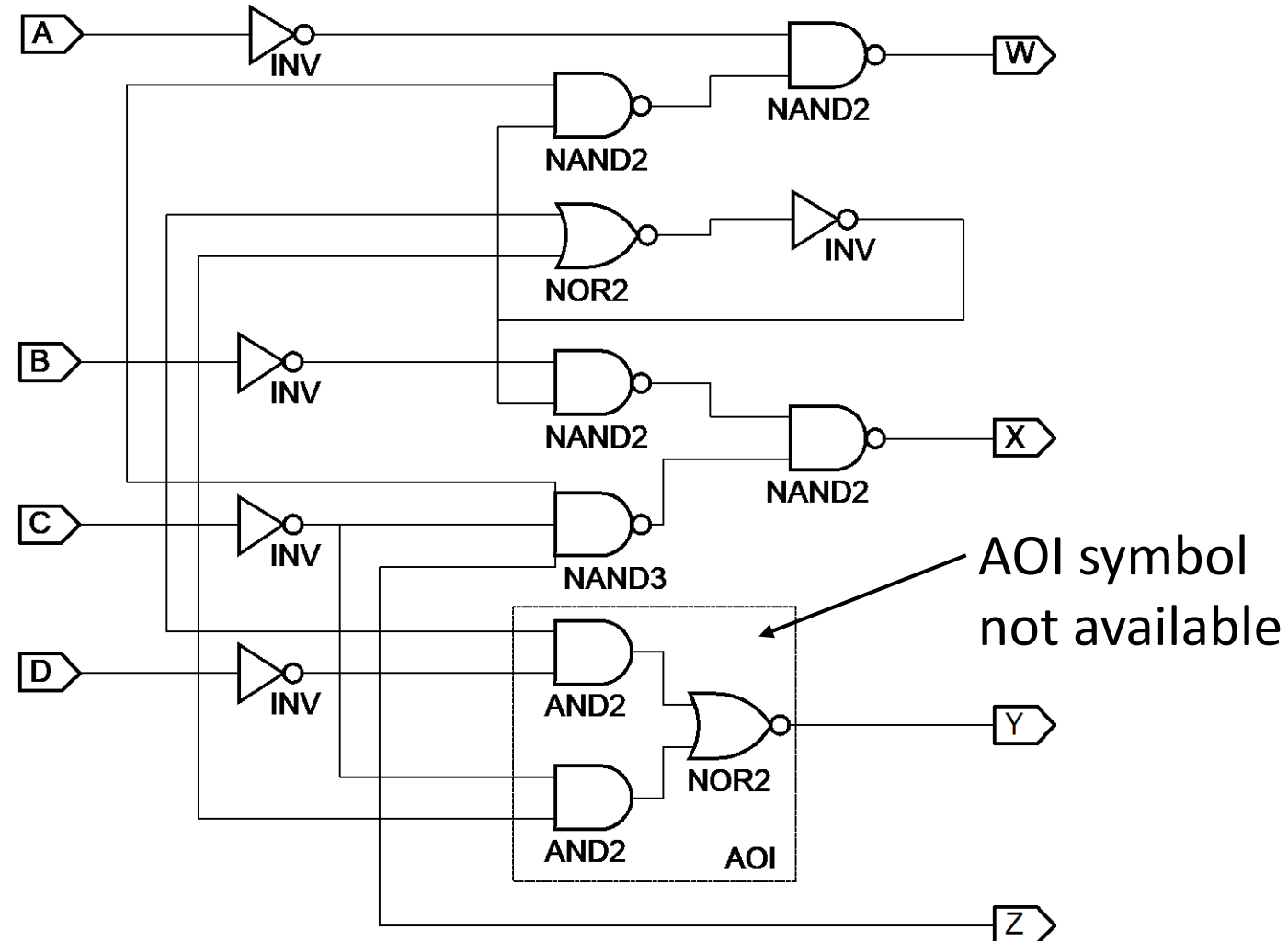
# Verification Example: Simulation




- Enter BCD-to-Excess-3 Code Converter Circuit Schematic


 
# Verification Example: Simulation



- Enter waveform that applies all possible input combinations:




- Are all BCD input combinations present? (Low is a 0 and high is a one)
 
# Verification Example: Simulation



- Run the simulation of the circuit for 120 ns



- Do the simulation output combinations match the original truth table?



□ 谢 谢！